

Digital Computer Organisation

Year 2010-2013

Answer Any Five Question

1. (a) Choose the correct options:
- I. The [art of machine level instruction, which tells the central processor what was to be done is _____
 - a) Operation code
 - b) Address
 - c) Operand
 - d) None of the above
 - II. Half adder consist of _____ & _____ Gates
 - a) EX-OR & AND
 - b) EX-OR & OR
 - c) EX-OR & NOT
 - d) None of these
 - III. Subtract $(1010)_2$ from $(1101)_2$ using 1st complement
 - a) $(1100)_2$
 - b) $(0011)_2$
 - c) $(1001)_2$
 - d) $(0101)_2$
 - IV. Full adder is constructed by using _____
 - a) Two Half Adder & one OR gate
 - b) Two OR gate & one HA
 - c) One HA & two OR gate
 - d) One OR gate & one HA
 - V. The digital system usually operated on _____ system
 - a) Binary
 - b) Decimal
 - c) Octal
 - d) Hexadecimal
 - VI. A logic gate is an electronic circuit which _____
 - a) Makes logic decisions
 - b) Allows electron flow only in one direction
 - c) Works on binary algebra
 - d) Alternates between 0 & 1 values
 - VII. The only function of a NOT gate is to _____
 - a) Stop a signal
 - b) Re-complement a signal
 - c) Invert an input signal
 - d) Act as a universal set

- VIII. Karnaugh map (K-map) technique provides a systematic method for simplifying_____
- Multiplexers
 - Logic gates
 - Boolean expressions
 - None of these
- IX. A register is a group of_____
- OR gates
 - OR &AND gates
 - Flip flops
 - None of these
- X. The NOT symbol at the output of an OR gate:
- Converts it into AND gate
 - Converts it into NAND gate
 - Converts it into XOR gate
 - Converts it into NOR gate

B. Fill in the blanks:

- _____is the name of the logic circuit which can add two binary digits.
 - The logical expression $(Y=A.B)$ is of _____gate
 - _____flip flop Considered the universal flip-flop.
 - A hexadecimal number system code uses _____ basic symbols.
- Briefly explain the reason that why we have to simplify the Boolean functions ? Write few advantages also.
 - What are multiplexers? Differentiate between multiplexers and demultiplexers.
 - Simplify following Boolean function using k-map:
 $F(A,B,C,D)=\Sigma(0,1,2,3,5,8,9,10)$
 - What do you mean by 'Flip-Flop'? Explain various Flip-flops along with their logic diagrams and truth tables.
 - Discuss the term 'Memory Hierarchy'. Write a note on 'Associative Memory'.
 - What do you mean by 'logic family'? Explain its characteristics.
 - List down various advantages of using a CPU register for temporary data storage over using a memory location?
 - Describe briefly the working of DMA Controller with suitable diagram.
 - Write short notes of any two from following:
 - Cache Memory
 - Data Transfer modes
 - Encoder-Decoder
 - Virtual Memory